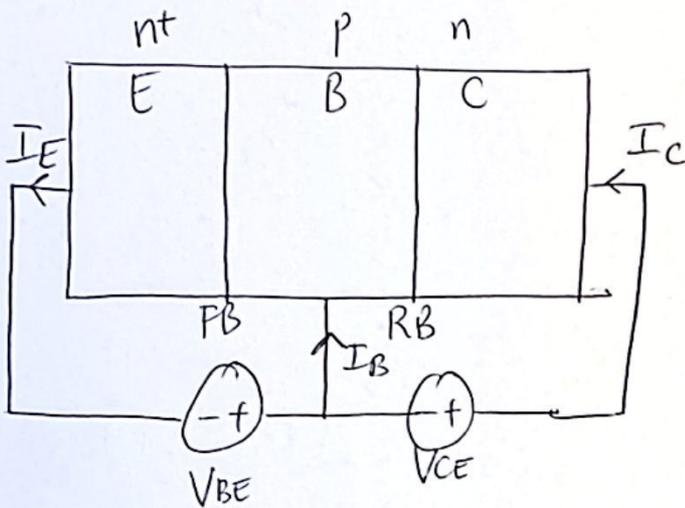


Lec 12 BJT Circuit Models

→ Large Signal Model


(1) Forward Active Region





$$I_E = I_{ES} (e^{\frac{V_{BE}}{V_T}} - 1)$$

$$I_C = \alpha_0 I_E$$

$$I_B = I_E - I_C$$

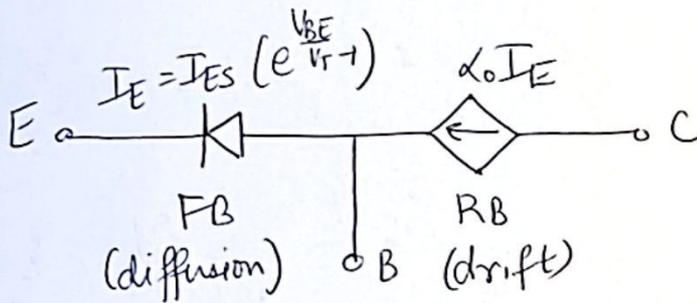


→ Simplest model "T-model"

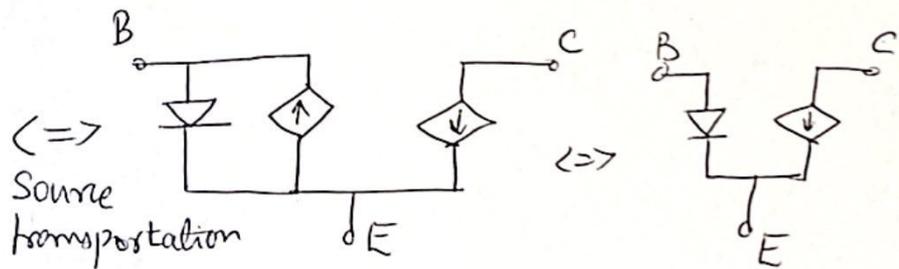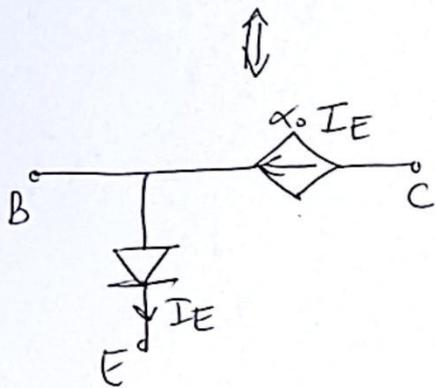

$$I_B = I_E - \alpha_0 I_E$$


"Pi-model"

② Reverse Active Region

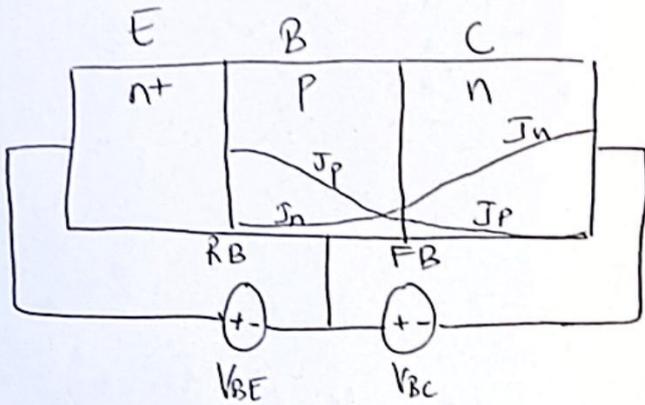

> Bad transistor since most electrons recombine in the base.


> β_0 is low & α_0 is also low.

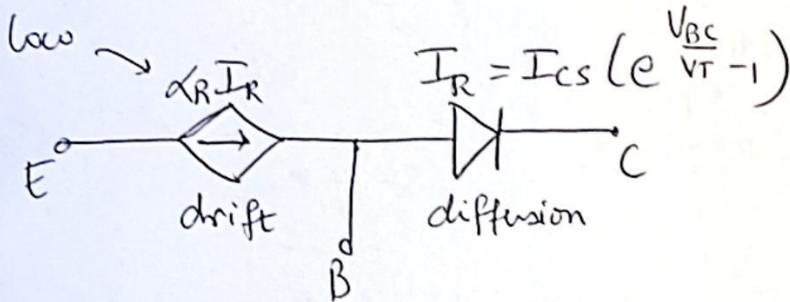

③ Cutoff : Both are reverse biased & no current flows!


④ Saturation : Both are FB & act like two back to back diodes.
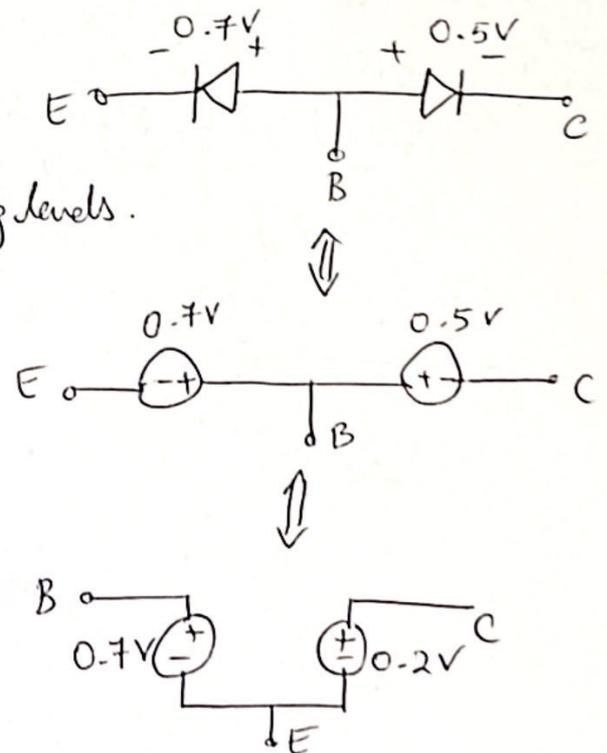
> 0.7V & 0.5V are forward voltages due to different doping levels.



Ebers Moll Model

> Combining all 4 operating regions,

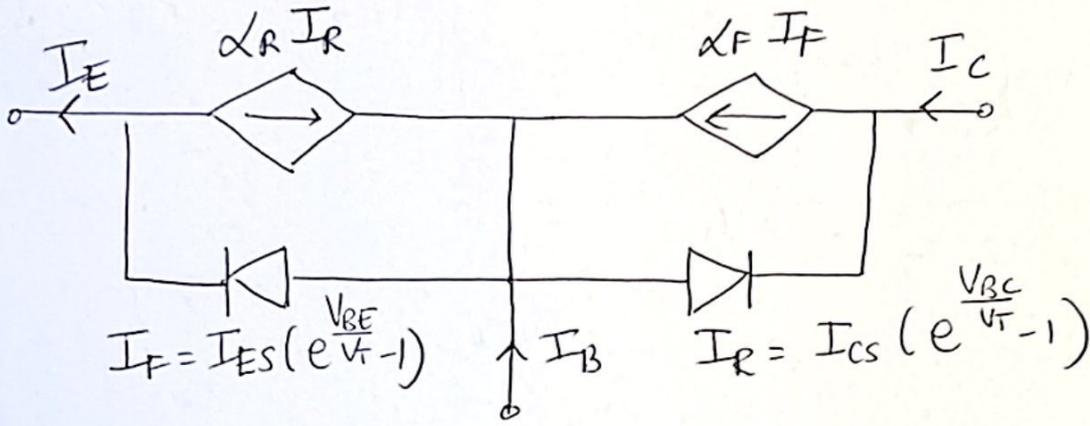


$$I_E = I_{ES} \left(e^{\frac{V_{BE}}{V_T}} - 1 \right) - \alpha_R I_{CS} \left(e^{\frac{V_{BC}}{V_T}} - 1 \right)$$

$$I_C = \alpha_F I_{ES} \left(e^{\frac{V_{BE}}{V_T}} - 1 \right) - I_{CS} \left(e^{\frac{V_{BC}}{V_T}} - 1 \right)$$

Base Width Modulation

> So far we have ignored the impact of V_{CE} on I_C .

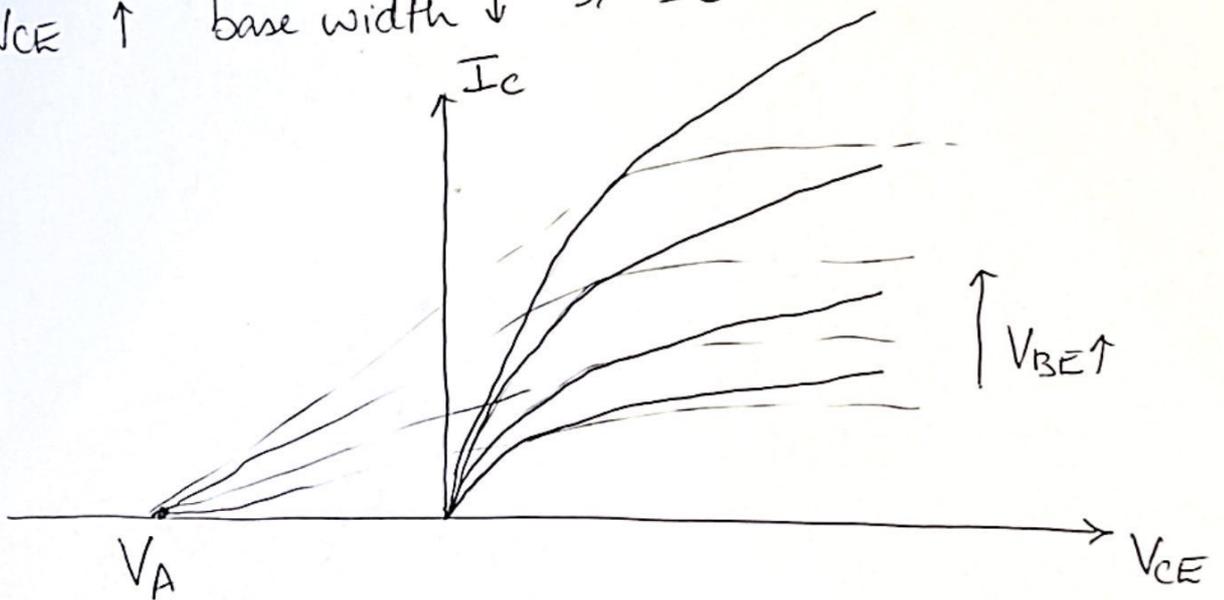When $V_{CE} \uparrow$ base width $\downarrow \Rightarrow I_C$ increases.



> V_A is an approximate point from which I_c slopes emerge.

> $V_A \rightarrow$ Early voltage (named after James Early).

$$\frac{I_c}{V_A} = \frac{\partial I_c}{\partial V_{CE}} \Rightarrow V_A = \frac{I_c}{\frac{\partial I_c}{\partial V_{CE}}}$$

$$\Rightarrow \boxed{I_c = I_s \left(e^{\frac{V_{BE}}{V_T}} - 1 \right) \left(1 + \frac{V_{CE}}{V_A} \right)} \rightarrow \begin{array}{l} \text{Valid in} \\ \text{Forward} \\ \text{Active} \end{array}$$


~~Ebers Moll Currents~~

~~$I_E = I_{ES} (e^{\frac{V_{BE}}{V_T}} - 1) - \alpha_R I_{CS} (e^{\frac{V_{BC}}{V_T}} - 1)$~~

~~$I_C = \alpha_F I_{ES} (e^{\frac{V_{BE}}{V_T}} - 1) - I_{CS} (e^{\frac{V_{BC}}{V_T}} - 1)$~~

Small Signal Model
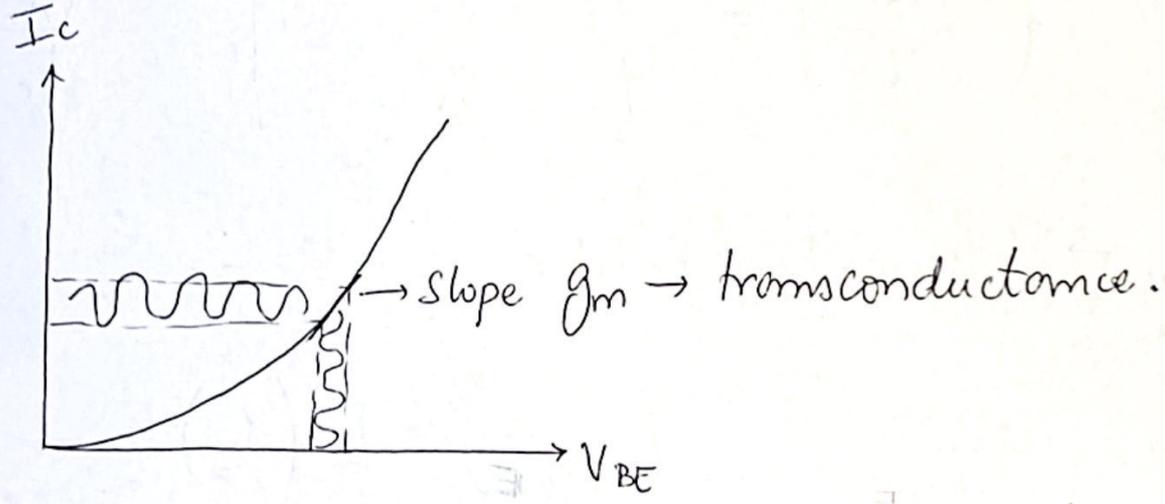
> We want to "linearize" the circuit model so we can apply linear circuit analysis (Superposition, Impulse Response)



$g_m = \frac{\partial I_C}{\partial V_{BE}} = \frac{\partial}{\partial V_{BE}} (I_S (e^{\frac{V_{BE}}{V_T}} - 1))$ {Ignoring B.W.M}

$g_m = \frac{I_C}{V_T} = \frac{1}{r_m} \rightarrow$ Main parameter.

$\Rightarrow \frac{i_c}{V_{be}} = \frac{\partial I_C}{\partial V_{BE}} = g_m$

Parasitics

① $r_{\pi} \Rightarrow$ Base Resistance

$$r_{\pi} = \left(\frac{\partial I_B}{\partial V_{BE}} \right)^{-1} = \beta_0 \left(\frac{\partial I_C}{\partial V_{BE}} \right)^{-1} = \frac{\beta_0}{g_m} = \beta_0 r_m$$

large!

② Base Width Modulation (r_o)

$$r_o = \left(\frac{\partial I_C}{\partial V_{CE}} \right)^{-1} = \left[\frac{I_S \left(e^{\frac{V_{BE}}{V_T}} - 1 \right)}{V_A} \right]^{-1} \approx \frac{V_A}{I_C}$$

③ $r_{\mu} \rightarrow$ Collector Base Resistor

$$r_{\mu} = \frac{\partial I_B}{\partial V_{CE}} = \beta_0 \left(\frac{\partial I_C}{\partial V_{CE}} \right)^{-1} \approx \beta_0 (r_o)$$

At $T = 300K$, $V_T = 25.8mV$, if $I_C = 1mA \Rightarrow g_m \approx 40mS$

Say $\beta = 100$, $V_A = 25V$

$$r_m = 25\Omega$$


$$r_{\pi} = \beta_0 r_m = 2.5k\Omega$$

$$r_o = \frac{V_A}{I_C} = 25k\Omega$$

$$r_{\mu} = \beta_0 r_o = 2500k\Omega = 2.5M\Omega$$

We want r_m to be small & r_{π}, r_o, r_{μ} to be large!

Small Signal Model

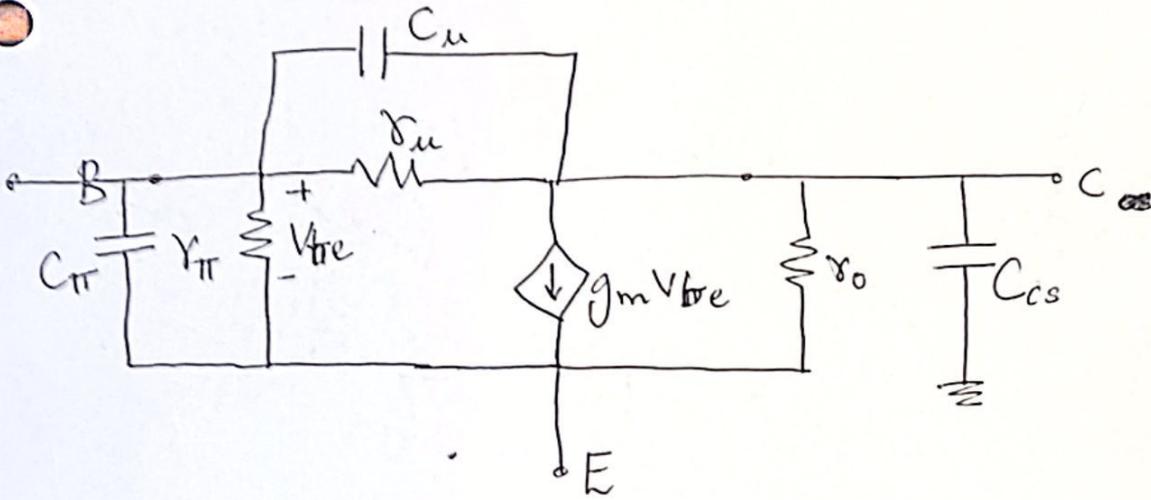


C_{π} & C_{μ} are junction capacitances.

C_{cs} is a capacitance between the collector & substrate.

$$g_m = \frac{I_c}{V_T}, \quad r_{\pi} = \frac{\beta_0}{g_m}, \quad r_o = \frac{V_A}{I_c}, \quad r_{\mu} = \beta_0 r_o$$

const.
const.
const.

Why do BJTs make a bad switch?

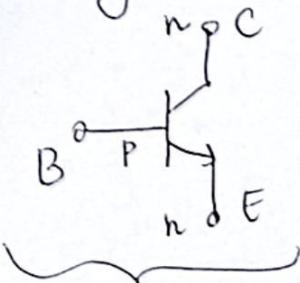

B pulled up \Rightarrow Sat & current flows
 \Rightarrow charge carriers are injected into Base from both E & C.

B pulled down \Rightarrow Cut off \Rightarrow Both junctions are RB. But electrons in base are drained into Collector & Emitter where they must recombine
 Storage is the problem which is slow or they must be removed with a current \Rightarrow BAD.

Minority carriers
 Storage is the problem
 \Downarrow
 MOSFET!